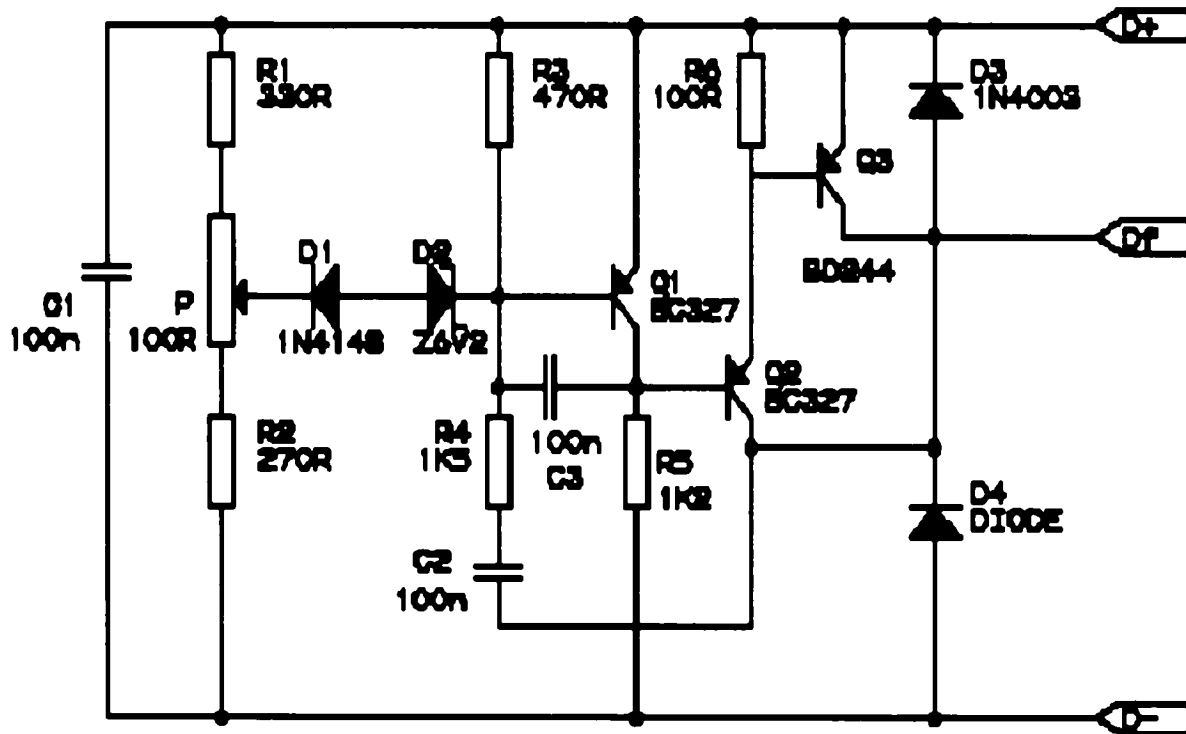


BMW R Series Motorcycle Regulator Schematic



PARTS:

R1 330
 R2 270
 R3 470
 R4 1.5K
 R5 1.2K
 R6 100
 P 100 ohm pot
 C1, C2, C3 100nF ceramic
 Q1, Q2 BC327
 Q3 BD244A
 D1 1N4148
 D2 BZX6V2 zener, 6.2V
 D3 1N4003

D4 no markings, but a 10A, 50V schottky should do the job here. Strangely enough, the diodes in my Siemens databooks that use this package go up to about 3A, which I consider a little low for this application (BY245, BY246).

From the wiring diagram in my manual:

D+

AdChoc:

Moto

Acces

Clothr

luggaç

to 50%

access

www.17

speci

rectif

made

silicon

seleni

OEM p

www.be

ROHM

regul

Efficie

skip cç

Offere

output

www.rot

DIY E

Schei

All Pro

Previe

10000

www.Eh

Ethyl

Respe

et rec

Ethyl

gratuit

Ethyl

Goes to output of diode board and alternator telltale.

Df

Goes to one end of alternator rotor.

D

Goes to the other end of the alternator rotor, and it may also go to bike ground through the case of the regulator.

Description:

Correctly adjusted, the voltage on the pot wiper is slightly less than half D+ (appx. $0.47 \cdot D+$) and Q1 will conduct if $(D+) - (V_p) > 6.2 + 0.7 + 0.7$, or $0.53 \cdot (D+) > 7.6V$, $(D+) > 14.3V$. If D+ is lower than 13.7V, Q1 will not conduct, Q2 will get driven via R5, and Q3 will conduct. Df will carry a voltage. When D+ rises, Q1 will start conducting, Q2 will get pinched gradually, and so will Q3. Voltage on Df will drop.

This was originally investigated by Matt Bennett, but the diagram, functional description, and many corrections were done by Rik Steenwinkel, rsteenw@ibm.net or rik@apd.dec.com.

Revised on 10/3/95 by Matt Bennett