

# An Analysis of the Split-Load Phase Inverter

GEORGE ELLIS JONES, JR.\*

A mathematical proof of the characteristics of the cathodyne phase inverter which has often been the subject of discussion as to its balance over the frequency range from lows to highs.

**D**ESIGNERS often avoid using the split-load phase inverter due to a rather widely held impression that its high-frequency response is very poor. Using but one triode, it has a very high input impedance and is readily balanced at low frequencies to give an over-all gain of slightly less than two.

Referring to Fig. 1, it may be seen that the prejudice against this inverter grows from the apparent differences in source impedance seen by the plate and cathode output loads. The cathode source impedance, being that of an amplifier with degenerative voltage feedback, is low. At the plate terminal an amplifier with degenerative current feedback is seen, and here the source impedance is high. The shunting effects of inverter tube capacitances, wiring capacitances, and input capacitances of the following stage are then supposed to reduce the high-frequency gain more rapidly at the plate than at the cathode terminal. However, since these capacitances shunt both terminals simultaneously, the actual situation is rather favorable.

Based on the preceding discussion, we may make the following analysis. Where:

$R_b$  = plate load resistance  
 $R_k$  = cathode load resistance  
 $r_p$  = dynamic plate resistance  
 $\mu$  = amplification factor  
 $A_{pg}$  = grid to plate gain  
 $A_{kg}$  = grid to cathode gain  
 $Z$  = source impedance

$$A_{pg} = \frac{-\mu R_b}{r_p + (\mu + 1)R_k + R_b}$$

$$A_{kg} = \frac{+\mu R_k}{r_p + (\mu + 1)R_k + R_b}$$

$$Z_p = r_p + (\mu + 1)R_k$$

$$Z_k = (r_p + R_b) / (\mu + 1)$$

$$R_b = R_k = R$$

$$A_{pg} = -A_{kg} = \frac{-\mu R}{r_p + (\mu + 2)R}$$

Often the two output terminals are shunted by approximately equal impedances. This will occur if the subsequent stage involves un-neutralized triodes so that their input capacitances

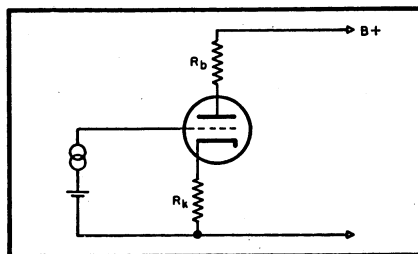


Fig. 1. Typical cathodyne split-load phase inverter circuit.

(which will be similar) make trivial the much smaller and mutually different wiring and inverter input capacitances.

$C_p$  = plate shunting capacitance

$C_k$  = cathode shunting capacitance

$C_p = C_k = C$

$X_c = 1/2\pi fC$

$$A_{pg} = \frac{-\mu \frac{R_b j X_c}{R_b + j X_c}}{r_p + (\mu + 1) \frac{R_k j X_c}{R_k + j X_c} + \frac{R_b j X_c}{R_b + j X_c}} \times \frac{1}{1 + \frac{r_p}{\mu + 2} R / \left( \frac{r_p}{\mu + 2} + R \right) j X_c}$$

$$= \frac{-\mu R}{r_p + (\mu + 2)R} \times \frac{1}{1 + \frac{r_p}{\mu + 2} R / \left( \frac{r_p}{\mu + 2} + R \right) j X_c}$$

$$A_{kg} = \frac{+\mu \frac{R_k j X_c}{R_k + j X_c}}{r_p + \frac{R_b j X_c}{R_b + j X_c} + (\mu + 1) \frac{R_k j X_c}{R_k + j X_c}} = \frac{+\mu R}{r_p + (\mu + 2)R}$$

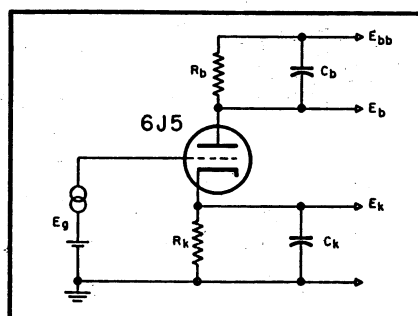


Fig. 2. Schematic of test set-up used to check calculations.

$$\times \frac{1}{1 + \frac{r_p}{\mu + 2} R / \left( \frac{r_p}{\mu + 2} + R \right) j X_c}$$

It is seen that the gain from grid to either cathode or plate output is identical, and with equivalent capacitances as would normally be encountered, the frequency response is the same at both outputs.

The high-frequency roll off will be the same for both plate and cathode outputs and the gain will be down 3 db from the mid-frequency value at:

$$f_o = \frac{1}{2\pi C \frac{r_p}{\mu + 2} R / \left( \frac{r_p}{\mu + 2} + R \right)}$$

To verify this derivation the experimental set-up shown in Fig. 2 was used.

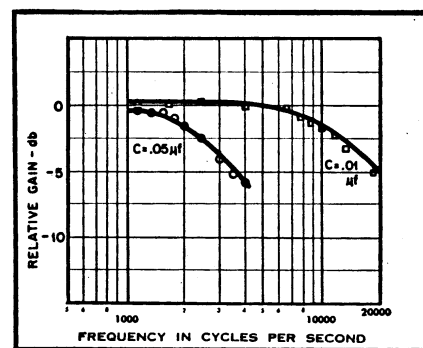


Fig. 3. Frequency response of test set-up under various conditions.

Relatively large values for  $C_k$  and  $C_p$  were inserted to minimize the unbalance created by the connection of test probes and also to bring the calculated 3 db frequency down to a convenient range.

Conditions of the experiment were as follows:

$E_{bb} = 255$  volts

$E_b = 165$  volts

$E_k = 96.5$  volts

$E_g = 92.5$  volts

$R_b = R_k = 68,000$  ohms  $\pm 10\%$  (matched)

$C_b = C_k =$  either  $0.05$  mfd or  $0.01$  mfd  $\pm 20\%$  (matched)

Inspection of tube handbook curves

[Continued on page 40]

\* Instructor, Chemical Engrg. Dept., The University of Pittsburgh, Pittsburgh 13, Pa.

since there are no modifications to the standard Magnecorder, it is obvious that this amplifier could be used for specific applications where its simplicity and compactness was desirable, yet the recorder can be brought back to the studio and used with the standard amplifier whenever necessary.

#### PARTS LIST

$C_1, C_2$	10-10-20/450-450-25, electrolytic
$C_3$	.0025 $\mu$ f, mica
$C_4, C_5$	.01 $\mu$ f, 600 v. paper
$C_6$	1000 $\mu$ f, 15 v. electrolytic, with insulating tube and mounting clip
$C_7, C_8, C_{10}$	40 $\mu$ f, 450 v. electrolytic
$C_9$	20 $\mu$ f, 450 v. electrolytic

$C_{11}$	.02 $\mu$ f, 150 v. hearing aid type, paper
$J_1$	Cannon XL-3-13 receptacle
$J_2$	Cannon XL-3-14 receptacle
$J_3$	Single-circuit jack
$J_4$	Jones S-408-AB receptacle
$J_5$	Jones S-406-AB receptacle
$L_1, L_2$	Choke, 8 H. at 40 ma. Thor-darson T-20C52
$LS$	4 $\times$ 6 in. loudspeaker, 3.2-ohm voice coil
$M$	VU meter, B scale, Simpson Model 45
$P_1$	Jones P-408-CCT cable plug
$R_1, R_2$	47,000 ohms, $\frac{1}{2}$ watt
$R_3$	3300 ohms, $\frac{1}{2}$ watt
$R_4$	1.0 meg, 1 watt
$R_5$	0.47 meg, 1 watt
$R_6$	1-meg volume control, audio taper
$R_7$	1800 ohms, $\frac{1}{2}$ watt

$R_8$	0.22 meg, $\frac{1}{2}$ watt
$R_9$	0.82 meg, 1 watt
$R_{10}$	0.22 meg, 1 watt
$R_{11}$	0.56 meg, $\frac{1}{2}$ watt
$R_{12}, R_{13}$	300 ohms, 5 watt, Ohmite Brown Devil
$R_{14}$	27,000 ohms, 1 watt
$R_{15}$	8200 ohms, 2 watt
$R_{16}, R_{17}$	270 ohms, $\frac{1}{2}$ watt
$R_{18}$	560 ohms, $\frac{1}{2}$ watt
$R_{19}$	3900 ohms, 1 watt
RECT	Federal 1016 Selenium Rectifier
$S_{1A-H}$	8-pole, 2-pos. wafer switch, Centralab 1418
$S_2$	DPST toggle switch
$T_1$	30/50,000 input transformer, shielded, Triad HS-5
$T_2$	Output transformer, secondary impedances 500, 15, 8, 2 ohms, UTC S-14
$T_3$	Power transformer, 300-0-300 v. at 90 ma.; 5 v. at 3 amps; 6.3 v. at 2.5 amps.

Case for amplifier

Langevin Remote Control Cabinet, Type 1-A

Case for power supply

Bud Minibox, CU-2109

## PHASE INVERTER

[from page 16]

indicate that:

$$\mu = 18$$

$$r_p = \text{from } 15,000 \text{ to } 20,000$$

$$f_o \approx 3,000 \text{ to } 4,000 \text{ cps } (C = 0.05 \text{ mfd})$$

$$f_o \approx 15,000 \text{ to } 20,000 \text{ cps } (C = 0.01 \text{ mfd})$$

With an input to the inverter grid of about 2 volts (rms) results, Tables I and II, were obtained and plotted in Fig. 3.

TABLE I

Frequency (cps)	Relative Gain in db	
	$C = .01 \mu$ f	$C = .05 \mu$ f
1090	0	-0.4
1350	0	-0.6
1550		-0.8
1740		-1.1
2000		-1.6
2400	0.1	-2.4
2950		-3.6
3400		-4.7
4000	-0.1	-5.9
6300	-0.5	
7600	-0.9	
8600	-1.1	
10000	-1.6	
11100	-2.1	
12300	-2.3	
14000	-2.8	
18400	-5.1	


TABLE II

Shunt Capacitance	"3-db" frequency	
	Calculated	Observed
.05 $\mu$ f	3200 - 4230	2700
.01 $\mu$ f	16000 - 21100	14200
200 $\mu$ f	$3 \times 10^8 - 4 \times 10^8$	no data

It was found that the high frequency roll off was the same for both cathode and plate terminals. The calculation using 200  $\mu$ f should be representative for the loading presented by a triode in the subsequent stage.

It is believed that these results are

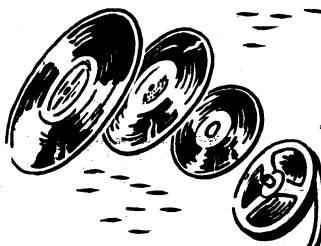**THEY ALL**  
*Sound*  
**BETTER WITH A**



# McIntosh

**WORLD'S FINEST AUDIO AMPLIFIER**


## 50 WATT AMPLIFIER

50 WATTS  
(peak: 100)  
50W-2  
\$249.50



Unequalled for  
quality reproduction  
of any sound source, the

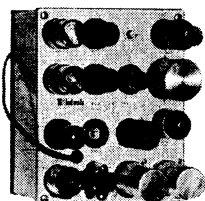McIntosh is the most advanced amplifier of the day. Its unique, compact design offers: **HIGHEST EFFICIENCY**—over 65%; **LESS THAN 1% DISTORTION AT PEAK POWER**; **DYNAMIC RANGE: OVER 70 db**; **FREQUENCY RESPONSE: 20-20,000 cps**.



20 WATTS (Peak: 40)  
20W-2 - \$149.50

AE-2 Amplifier  
Equalizer - \$74.50



SEND FOR *Free* CATALOG Dept. A-5

**McINTOSH ENGINEERING LABORATORIES, Inc.** 320 WATER STREET  
BINGHAMTON, N.Y.

valid only when the peak a.c. grid signal is of the less magnitude than the quiescent grid bias since greater excitation will tend to cut off the inverter tube, making the dynamic plate resistance infinite. However, when loaded with substantially equal impedances and driven at a relatively low level, the high-frequency roll-off of this inverter is about the same as that of a cathode follower; and the roll-off is the same for both plate and cathode terminals.

## INTERMODULATION TESTING

[from page 23]

with the generator section in Fig. 5. The low frequency, 60 cps, was chosen for convenience; it is believed sufficiently low to give an accurate check on amplifiers with output transformers of known high quality. This frequency is taken from one plate of the rectifier tube and dropped to a value of slightly over 3 volts, maximum, through a filter to reduce the higher harmonics in the line voltage. The 4000-cps oscillator uses a 6J5 triode and a tapped coil. A 150-mh r.f. choke will tune over a considerable range with a tap soldered at about one third out from center. The selector switch is set on 60 cy and a suitable voltage reading taken at the output terminals. Resistor  $R_7$  is then adjusted so as to give the same voltage after switching to 4 kc. If desired, a 'scope can be used, but the foregoing is simple and accurate. Resistor  $R_9$  across two contacts on the selector switch is for the purpose of setting the 4/1 ratio. CAUTION: The output potentiometer must be in the circuit at all times when these adjustments are made. The selector switch loads the circuit to the same extent in all positions, if connected as shown. The oscillator output can be adjusted over a wide range by means of the bias resistor. The generator as shown, will provide slightly over three volts of mixed signal. The separate 60- and 4000-cps cycle signals are convenient for general testing, and for checking the analyzer.

### Analyzer Section

In the analyzer portion of the instrument a level control is used for setting the carrier to a predetermined equivalent of 100 per cent and is connected to the input jacks, as shown in Fig. 6. These pin type jacks are located adjacent to the generator output jacks so that the analyzer may be checked for operation by means of one short piece of bus bar bent to bridge both upper jacks. The large knob is used for selecting the appropriate functions. The voltmeter circuit used is sufficiently linear to warrant the assumption that it is so. It will read input levels of 5, 10, 25 and 50 volts, full scale, and was calibrated against an r.m.s. meter. The particular meter used, in the circuit shown, reads 0.25 volts, full scale, with the signal applied to the grid of the associated section of the 12AT7 tube. The right section of the selector switch permits measuring full

# MAKING BOOSTER HISTORY THE TV-1



THE Turner Television Booster Model TV-1 has been on the market for less than a year, but already is making booster history. Reports from fringe areas all over the country are loud in their praise of the consistently superior performance of the TV-1. Wherever boosters are compared the Turner TV-1 produces the sharpest, clearest picture... the crisp, natural sound TV viewers seek.

Turner's advanced electronic engineering, plus solid, quality construction make the difference. The low-noise-level Cascode circuit stabilizes the picture, reduces noise and snow to a minimum, and produces an excellent picture under fringe area receiving conditions that nullify the best efforts of many other boosters.

Single knob continuous tuning permits fine adjustment for best possible reception of both picture and sound. Three position control switch turns on TV set only, TV set and booster, or shuts off both set and booster. The TV-1 also may be used to amplify FM, mobile and aviation radio signals.

The unit is quickly and easily installed. Attaches to any television set. Attractive styling and neutral finish harmonize with any furniture design.

Contact your Turner representative or write direct.

List price-----\$57.50

For the best possible TV reception, turn to

# THE TURNER BOOSTER

## THE TURNER COMPANY

000 17th Street N.E., Cedar Rapids, Iowa

IN CANADA:

Canadian Marconi Co.,  
Toronto, Ont., and Branches

EXPORT:

Ad. Auriema, Inc.,  
89 Broad Street, New York 4